

Name:

Period:

Date:

## Ohm's Law Calculations

In your own words, state the relationship between voltage, resistance and current in a circuit.

What happens to the current in a circuit if a 1.5-volt battery is removed and is replaced by a 9-volt battery?

How much current is in a circuit that includes a 9-volt battery and a bulb with a resistance of 3 ohms?

A circuit contains two 1.5 volt batteries and a bulb with a resistance of 3 ohms. Calculate the current.

What is the voltage of a circuit with 15 amps of current and toaster with 8 ohms of resistance?


A light bulb has a resistance of 4 ohms and a current of 2 A. What is the voltage across the bulb?

How many ohms of resistance must be present in a circuit that has 120 volts and a current of 10 amps?

You have a large flashlight that takes 4 D-cell batteries. If the current in the flashlight is 2 amps, what is the resistance of the light bulb? (Hint: A D-cell battery has 1.5 volts.)

Use the diagram to the right to answer the following problems.

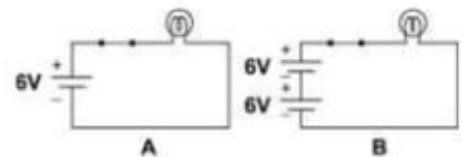- What is the total voltage in each circuit?
- How much current would be measured in each circuit if the light bulb has a resistance of 6 ohms?
- Is the bulb brighter in circuit A or circuit B? Why?



Name:

Period:

Date:

A voltage of 80 volts is applied to a resistor and the current going through is found to be 200 mA.

a) Convert the current to Amperes.

Answer \_\_\_\_\_ A

b) Calculate the **resistance** of the resistor.

Answer \_\_\_\_\_  $\Omega$

A kettle operates from a 120 V outlet. It has a heating element with a resistance of 8.0  $\Omega$ . Calculate the **current** going through the element.

Answer \_\_\_\_\_ A

A certain electric stove has a 16  $\Omega$  heating element. (The resistance is 16  $\Omega$ .) The current going through the element is 15 A. Calculate the **voltage** across the element.

Answer \_\_\_\_\_ v

In a small mp3 player, the current going through a 1800  $\Omega$  resistor is 1.67 mA.

a) Convert the current into Amperes.

Answer \_\_\_\_\_ A

b) Calculate the **voltage** across the resistor.

Answer \_\_\_\_\_ v